

## Interfacing Analog to Digital Data Converter: (ADC)

→ We can interface 8 bit and 12 bit analog to digital converter with 8086.

→ We use P20 8255 can be used to interface ADC & with 8086 microprocessor

→ The ADC is treated as an input device by the microprocessor, that sends an initializing signal to ADC to start the analog to digital conversion process.

→ The start of conversion signal is a pulse of a specific duration.

The process of A/D conversion is a slow process and the microprocessor has to wait for the digital data till the conversion is over.

After the conversion is over, the ADC sends end of conversion (EOC) signal to inform the microprocessor about it and the result is ready at the output buffer of ADC.

→ Three ~~that~~ tasks of issuing an SOC signal to ADC, and reading EOC signal from ADC and reading the digital output of the ADC are carried out by the CPU using 8255 I/O ports.

→ The time taken by the ADC from the active edge of SOC pulse till the active edge of EOC pulse is called as the conversion delay of ADC.

It may range anywhere from a few microseconds, in case of fast ADCs, to even a few hundred milliseconds in case of slow ADCs.

→ The selection of ADC required for a particular application is done, depending on required speed, resolution and cost factor.


→ The available ADCs in the market use different techniques for the conversion of analog signals to digital signals. Successive approximation and dual slope integration techniques are the most popular techniques used in integrated ADC chips.

→ A general algorithm for interfacing an ADC contains the following steps:


- ① Ensure the stability of analog input, applied to the ADC.
- ② Issue start of conversion (SOC) pulse to ADC.
- ③ Read end of conversion (EOC) pulse to mark the end of conversion process.

## ADC 0808/0809 :

- The ADC chips 0808/0809 are 8 bit CMOS, successive approximation converters.
- Successive approximation is one of the fastest technique used for the process of analog to digital conversion.
- The conversion delay is  $100\mu s$  at a clock frequency of  $640kHz$ , which is quite low as compared to other converters.
- These converters do not need any external zero or full scale adjustments as they are taken care by internal circuits.

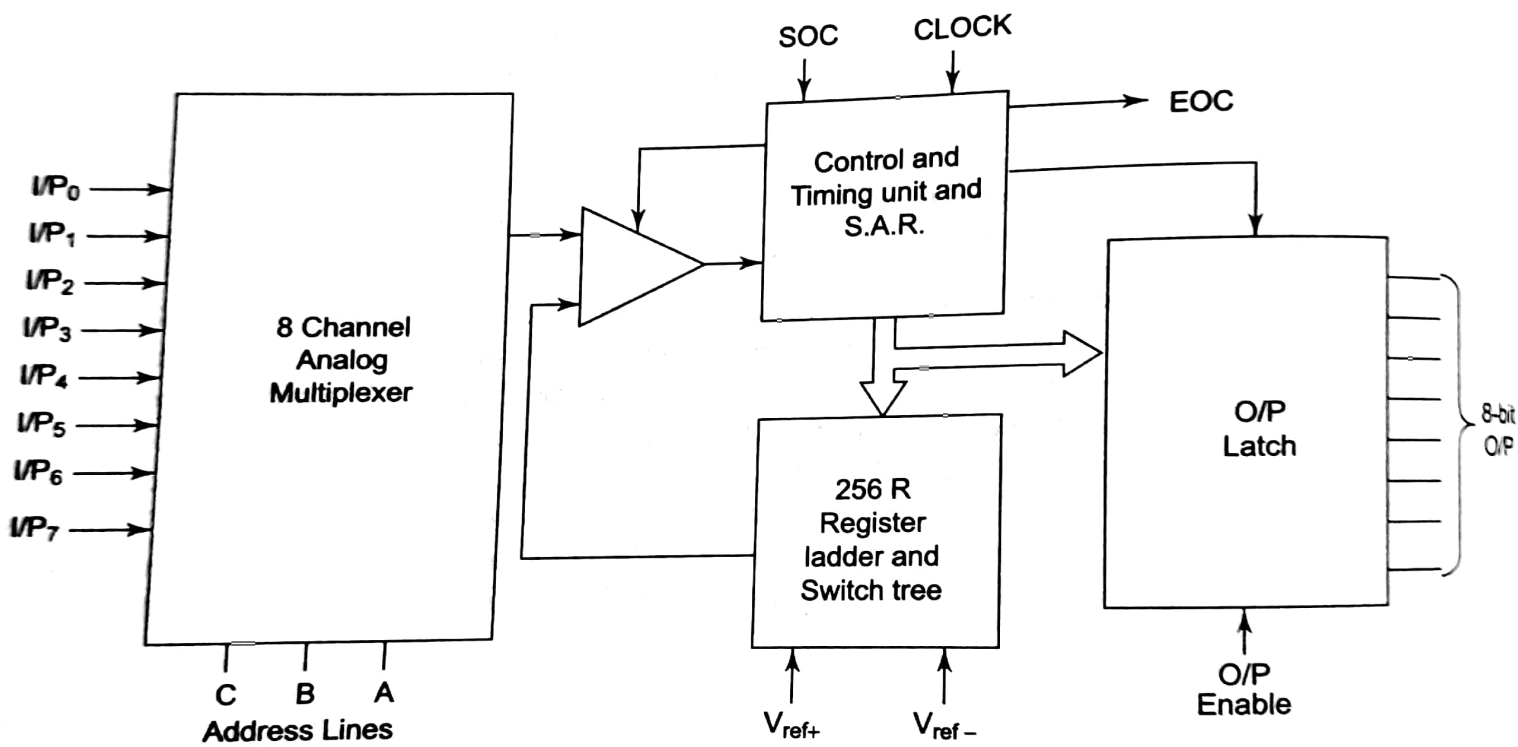

**Fig. 5.37(a) Block Diagram of ADC 0808/0809**

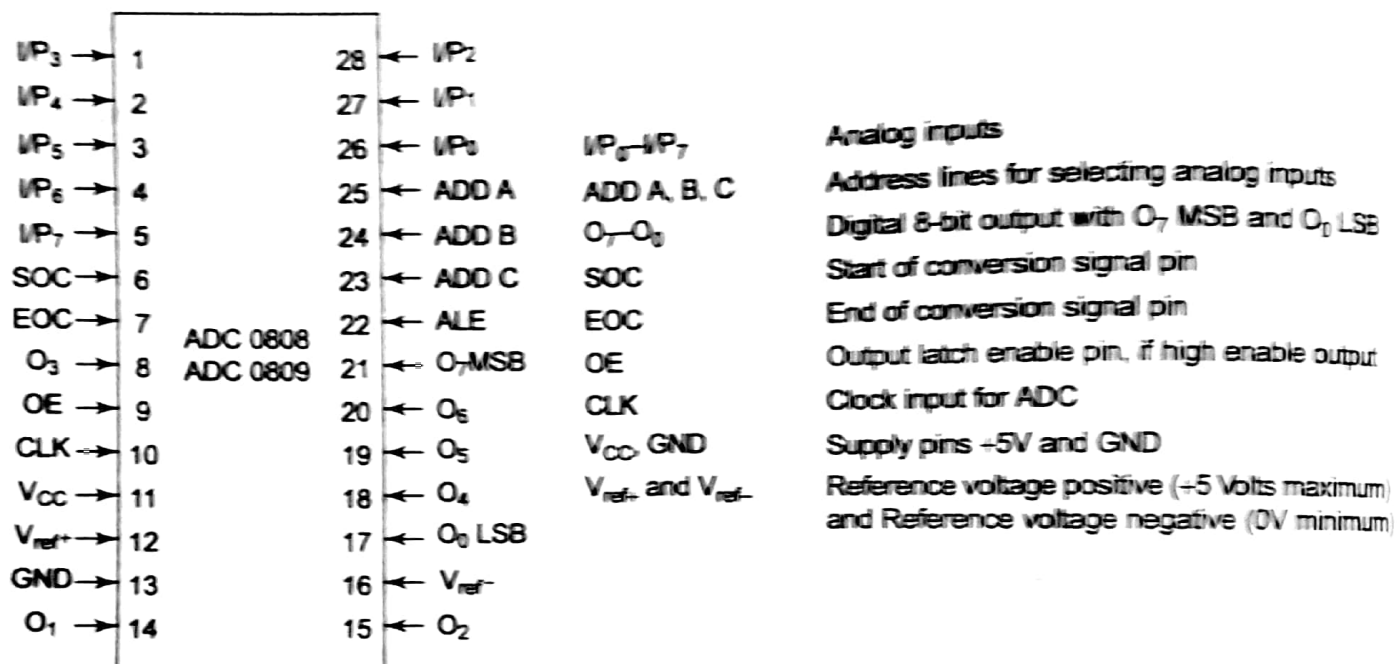

**Fig. 5.37(b) Pin Diagram of ADC 0808/0809**

→ These converters have a 3:8 analog multiplexers so that at a time eight different analog inputs can be connected to the chips.

Out of these eight inputs, only one can be selected for conversion by using address lines ADD A, ADD B and ADD C as shown.

The CPU can drive these lines using output port ~~the~~ lines in case of multichannel applications.

In case of single input applications, these may be hardwired to select proper input.

Analog Z/P selected	Address lines		
	C	B	A
Z/P 0	0	0	0
Z/P 1	0	0	1
Z/P 2	0	1	0
Z/P 3	0	1	1
Z/P 4	1	0	0
Z/P 5	1	0	1
Z/P 6	1	1	0
Z/P 7	1	1	1

→ These are unipolar ADC i.e. they are able to convert only positive analog input voltages to their digital equivalents.

→ These chips do not contain any internal sample and hold circuit.

If one needs a sample and hold circuit for conversion of fast signals into equivalent digital quantities, it has to be externally connected at each of the analog inputs.



Ques  
Interface ADC 0808 with 8086 using 8255 ports.

Use Port A of 8255 for transferring digital data output of ADC to the CPU and port C for control signals.

Assume that analog input is present at  $IP_2$  of ADC and a clock input of suitable frequency is available for ADC.

Draw the schematic and write the required ALP.

Sol

The analog input  $IP_2$  is used and therefore address pins ABC should be 010 respectively to select  $IP_2$ .


The OE and ALE are already kept at +5V to select ADC and enable the output.

Port C upper acts as input port to receive

EOC signal.

Port C lower acts as output port to send SOC signal to ADC.

Port A acts as 8-bit input data port to receive digital data output from ADC.

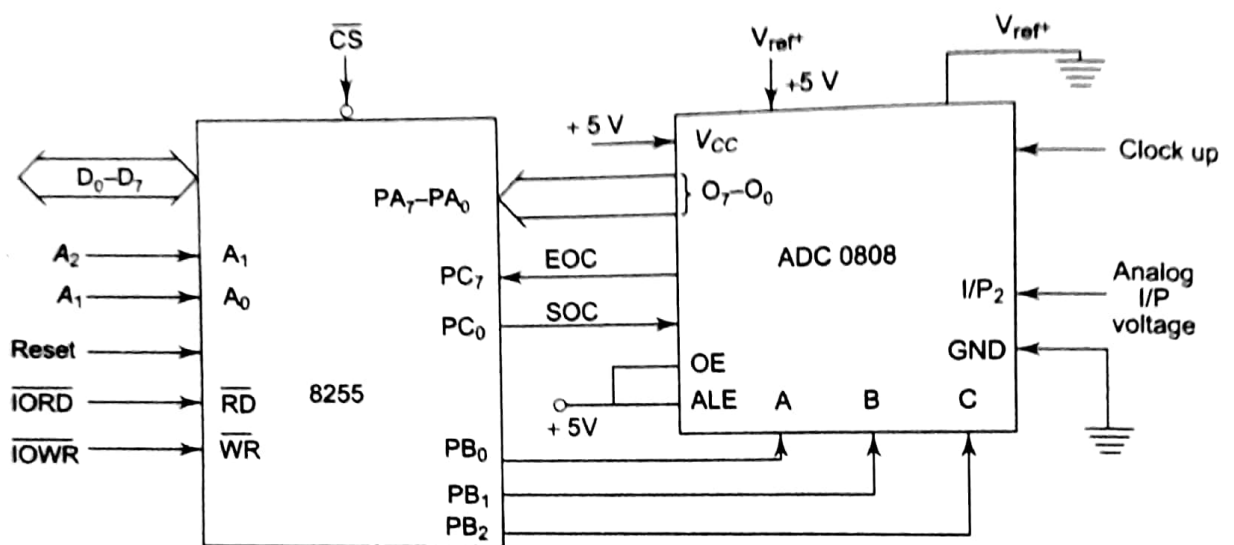

**Fig. 5.39** Interfacing 0808 with 8086

**Solution** Figure 5.39 shows the interfacing connections of ADC0808 with 8086 using 8255. The analog input  $I/P_2$  is used and therefore address pins A,B,C should be 0,1,0 respectively to select  $I/P_2$ . The OE and ALE pins are already kept at +5V to select the ADC and enable the outputs. Port C upper acts as the input port to receive the EOC signal while port C lower acts as the output port to send SOC to the ADC. Port A acts as a 8-bit input data port to receive the digital data output from the ADC. The 8255 control word is written as follows:

D <sub>7</sub>	D <sub>6</sub>	D <sub>5</sub>	D <sub>4</sub>	D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>	Control word
1	0	0	1	1	0	0	0	= 98 H

The required ALP is given as follows:

```

MOV AL,98 H           ; Initialise 8255 as
OUT CWR,AL           ; discussed above
MOV AL,02H           ; Select I/P2 as analog
OUT PORT B,AL        ; input
MOV AL,00H           ; Give start of conversion
OUT PORT C,AL        ; pulse to the ADC.
MOV AL,01 H          ;
OUT PORT C,AL        ;
MOV AL,00H           ;
OUT PORT C,AL        ;
WAIT : IN AL,PORTC    ; Check for EOC by
RCL                  ; reading port C upper and
JNC WAIT             ; rotating through carry.
IN AL,PORTA          ; If EOC, read digital equivalent in
                    AL
HLT                  ; Stop

```


**Program 5.11** ALP for Problem 5.16

## Interfacing Digital to Analog converter (DACs) :

- The DAC converts binary numbers into their equivalent analog voltage.
- The DAC finds applications in areas like digitally controlled gains, motor speed controls, programmable gain amplifiers etc.

## AD ~~7523~~ <sup>7523</sup> 8 bit multiplying DAC :

- Interdual <sup>7523</sup> AD ~~7523~~ is a 16 pin DIP, multiplying DAC, containing R-2R ( $R=10k$ ) for digital to analog conversion along with single pole double throw NMOS switches to connect digital inputs to the ladder.
- Supply range  $+5V$  to  $+15V$ .  
V<sub>ref</sub> can be between  $-10V$  to  $+10V$ .
- max. Analog o/p voltage =  $+10V$  when all digital inputs are at logical 1 state.
- A Zener diode is connected between OUT1, OUT2 to save DAC from negative transients.
- An Op Amp is need as a current to voltage converter at the o/p of AD ~~7523~~ <sup>7523</sup> to convert current o/p of AD ~~7523~~ <sup>7523</sup> to o/p voltage.

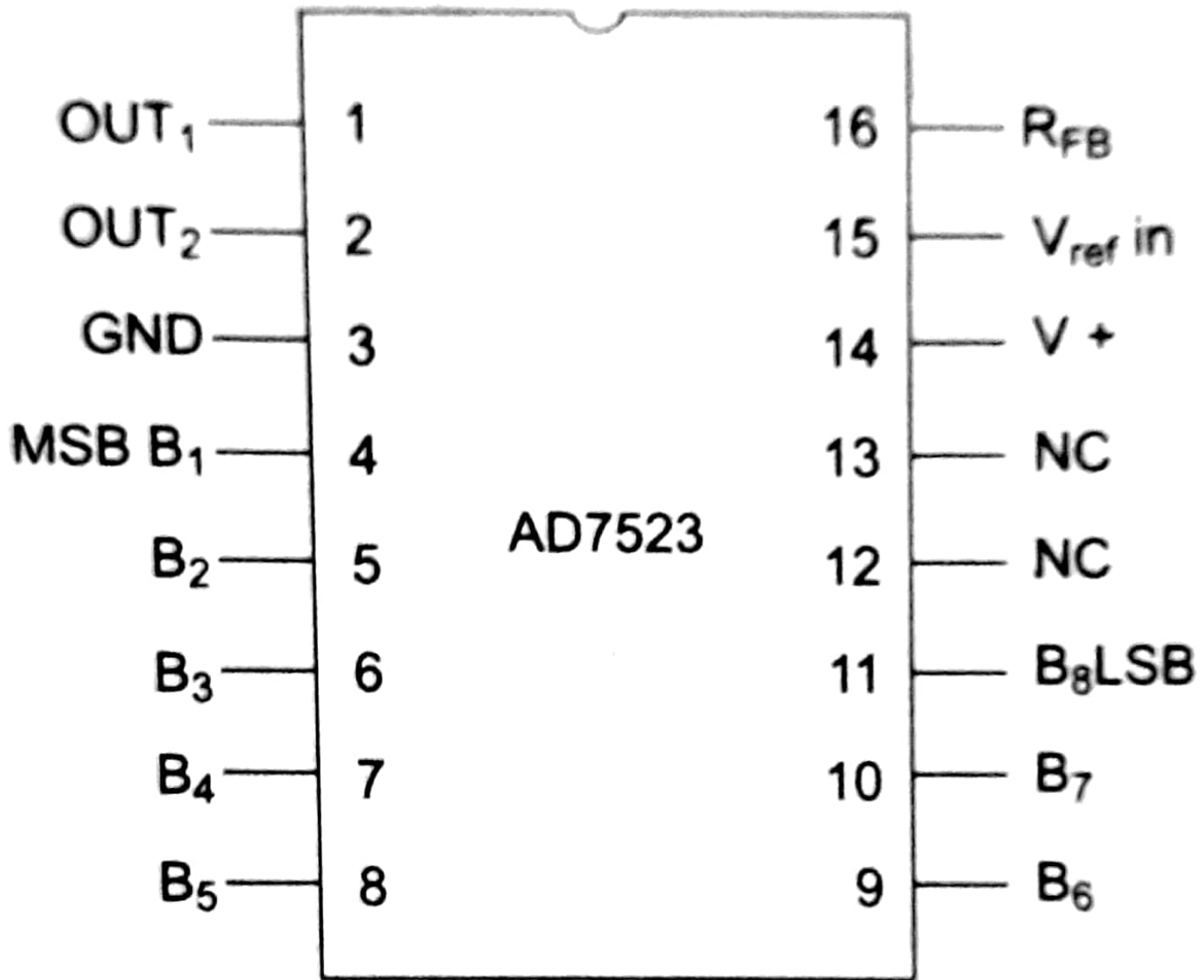

**Fig. 5.45** Pin Diagram of AD7523

Ex:-

Interface a DAC AD7523 with an 8086 CPU running at 8MHz and write an ALP to generate a saw-tooth waveform of period 1ms with V<sub>max</sub> 5V.

sl

ALP :

ASSUME CS : CODE

CODE SEGMENT

START : MOV AL, 80H ; port A as o/p port  
OUT CWR, AL ;

AGAIN : MOV AL, 00H ; start the ramp from 0V

BACK : OUT PORTA, AL ; o/p 00H to DAC

INC AL

COMP AL, 0F2H ; Is upper limit reached?

JB BACK ; If not, increment the ramp

JMP AGAIN ; else start again from 00H


CODE ENDS

END START

- port A is initialized as output port for sending digital data as input to DAC.
- The ramp starts from 0V (analog), hence AL starts at 00H.
- To increment the ramp, the content of AL is incremented during execution of the loop till it reaches F2H.
- After that ramp starts again from 00H i.e. 0V (analog) and procedure is repeated.
- The ramp period given by this program is precisely 1.000625ms.

Count F2H is calculated by dividing the required delay of 1ms by the time required for execution of the loop once.



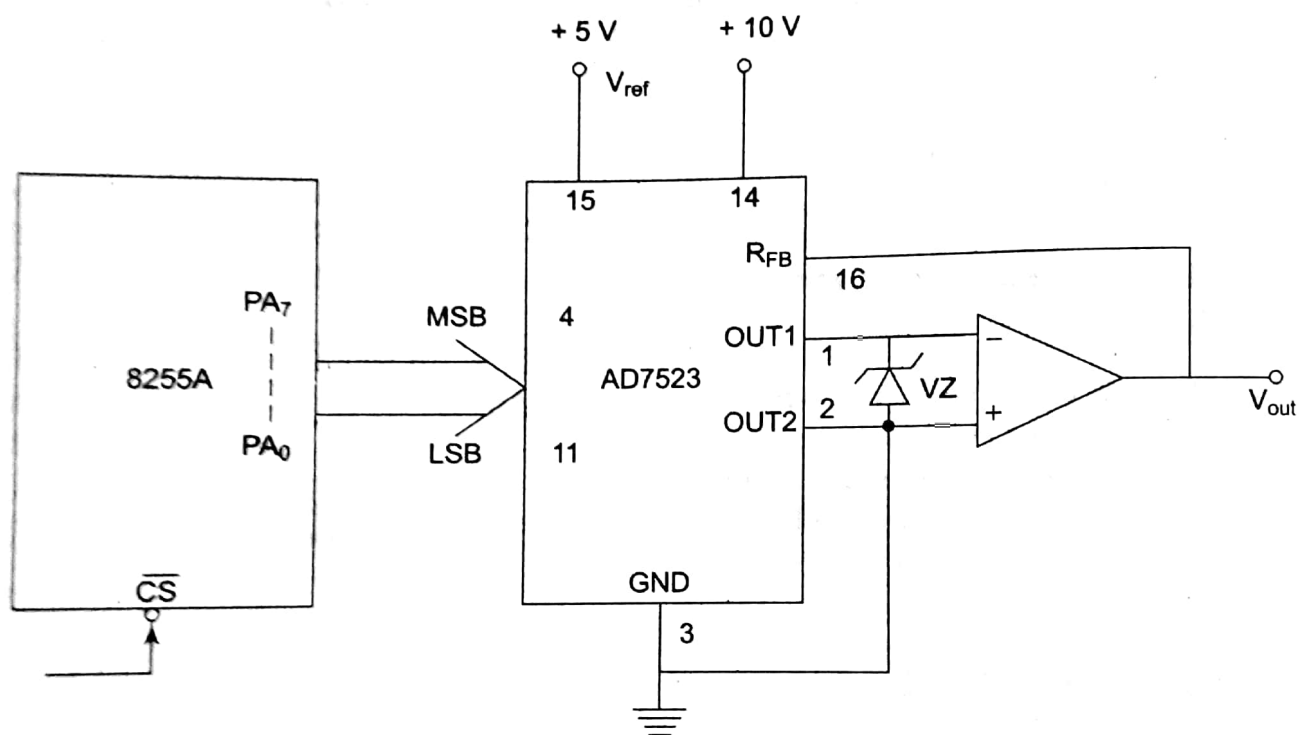

**Fig. 5.46** Interfacing of AD7523

```

CODE      SEGMENT
START:    MOV AL,80 H           ; Initialise port A as output
          OUT CWR,AL           ; port
AGAIN:    MOV AL,00H           ; Start the ramp from 0V
BACK :    OUT PORTA,AL         ; Input 00H to DAC
          INC AL               ; Increment AL to increase ramp output
          CMP AL,0F2H          ; Is upper limit reached?
          JB BACK              ; If not, then increment the ramp
          JMP AGAIN            ; Else start again from 00H
CODE      ENDS
          END START

```

**Program 5.13** ALP for Generating Sawtooth Waveform Using AD 7523


## DAC 0800 8 bit Digital to Analog converter:

→ The DAC 0800 is a monolithic 8 bit DAC manufactured by National Semiconductor.

→ It has settling time around 100ms and can operate on a range of power supply voltages i.e. from 4.5V to 18V.

→ Usually supply voltage  $V_{+}$  is 5V or +12V.


The  $V_{-}$  pin can be kept at a minimum of -12V.

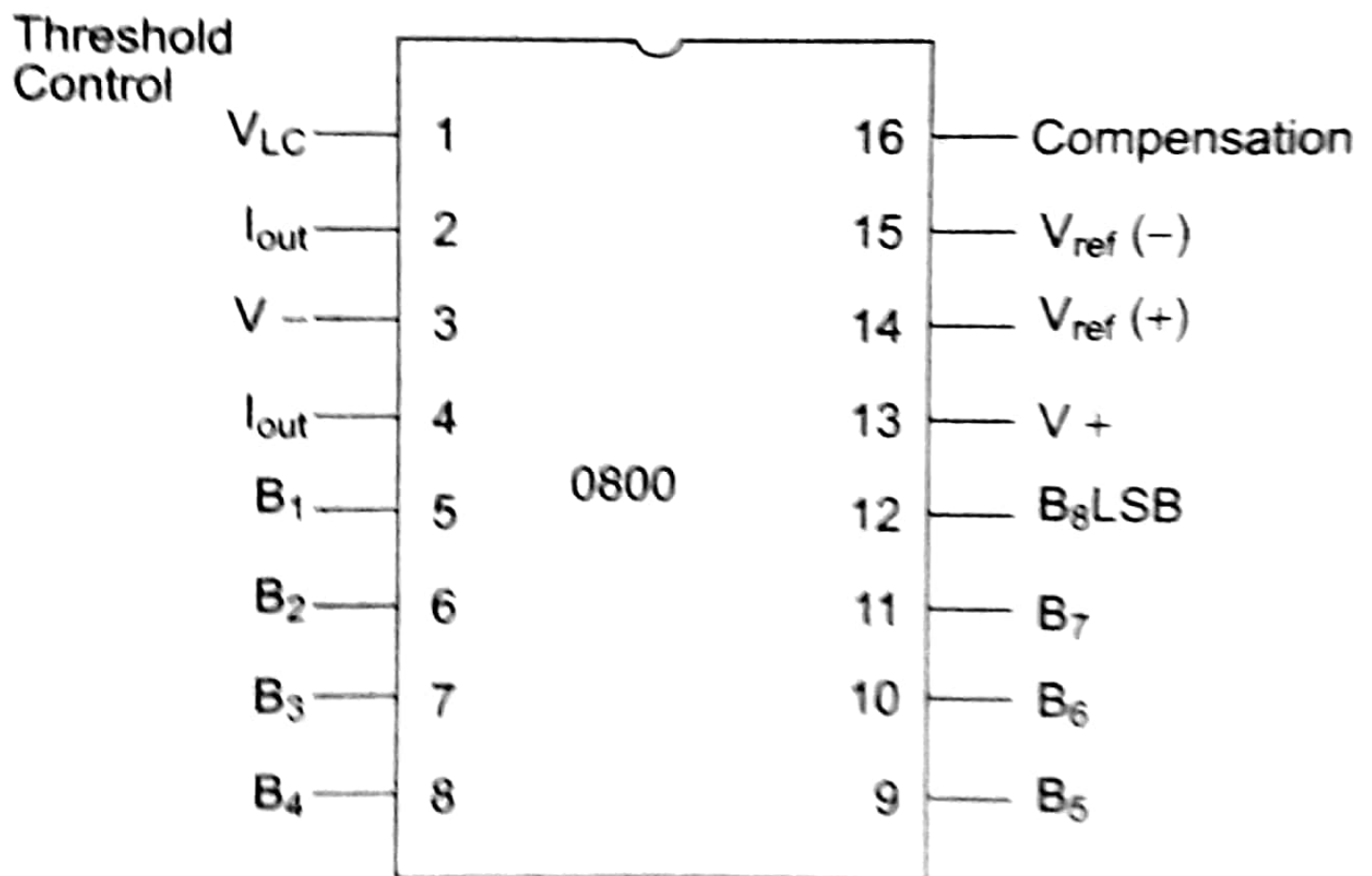

**Fig. 5.47** Pin Diagram of DAC 0800

Q. Write an ALP to generate a triangular wave of freq 500Hz using the interfacing circuit below. The 8086 operates at 5MHz. The amplitude of triangular wave should be +5V.

- Ans
- The  $V_{ref}+$  should be tied to +5V to generate a wave of +5V amplitude.
  - The required frequency of ~~input~~<sup>output</sup> is 500Hz. i.e. period is 2ms.
- Assuming the wave generated is symmetric, the waveform will rise for 1ms and fall for 1ms.
- This is repeated continuously.

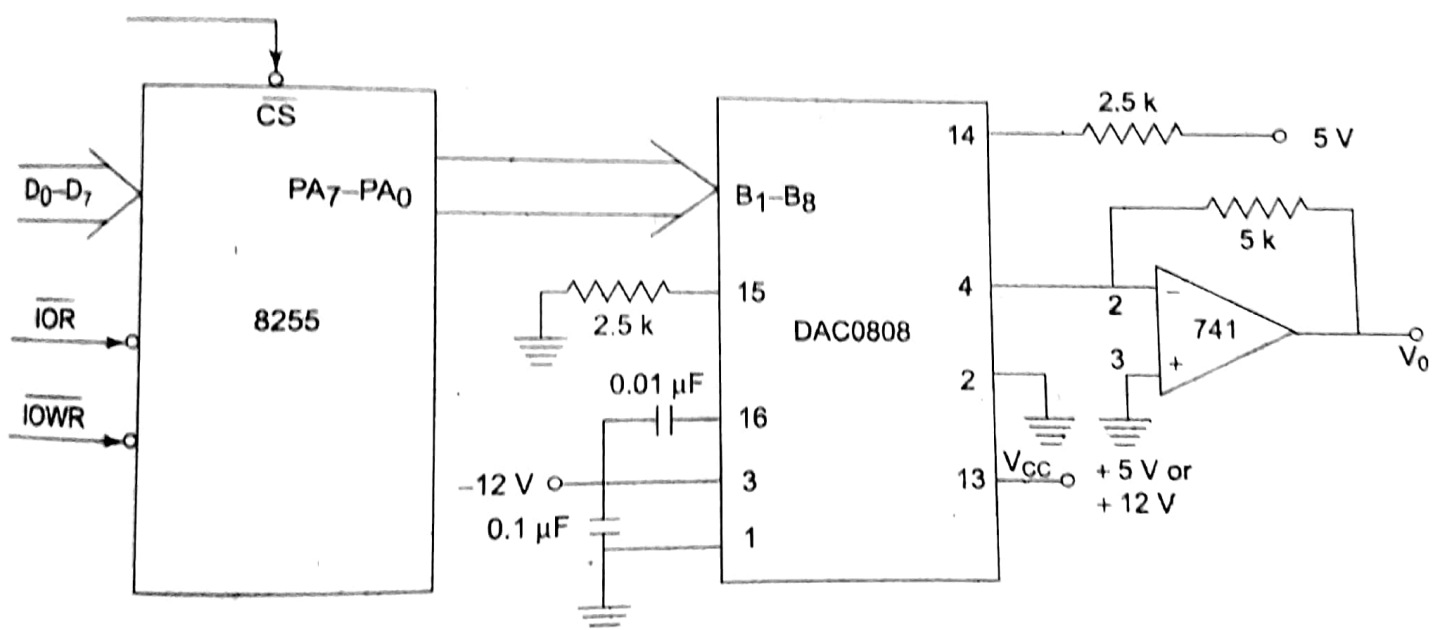

**Fig. 5.48** Interfacing DAC0800 with 8086

ALP

```
ASSUME CS: CODE
CODE SEGMENT
START:  MOV AL, 80H ; Init- 8255 port
        OUT CWR, AL ;
        MOV AL, 00H ; start rising ramp from
                     ; 0V by sending 00H to
                     ; DAC
BACK:   OUT PORTA, AL ;
        INC AL
        CMP AL, FFH ; If it is FFH then
BACK1:  OUT PORTA, AL ; output it and
        DEC AL        ; start the falling ramp
                     ; by decrementing AL
        CMP AL, 00    ; till it reaches 0.
        JN BACK1
        JMP BACK ; Then start again
                 ; for next cycle

CODE ENDS

END START.
```